

Lab 3

Alistair Morris
morrisa5@scss.tcd.ie

Semester II (2016)

1 Implementing a Boolean function

Implement a digital logic system that satisfies the following:

- $F = \sum m(1, 4, 5, 11, 12, 14, 15)$
- Note: $\sum md(2, 3, 7, 9)$ (don't cares)

Hints:

- Use a Karnaugh-map
- Try to find the lowest *Literal Count*